

# JSUNIL TUTORIAL

PANJABI COLONY GALI 01, SAMASTIPUR

## ASSIGNMENT

### Numerical on Current Electricity

- Q. 1.** Find the work done by an electron to maintain the potential difference of 80V?
- Q. 2.** What is the potential difference between the ends of  $16\Omega$  resistance, when a current of 1.5A flows through it?
- Q. 3.** The potential difference across the terminals of an electric iron is 240V and the current is 6 A what is the resistance of electric iron?
- Q. 4.** If there are  $10^8$  electrons flowing across any cross section of a wire in 4 minutes, what is the current in the wire?
- Q. 5.** A copper wire has diameter 0.5mm and resistivity  $1.6 \times 10^{-8}$  ohm m what will be the length of this wire to make the resistance of 10 ohms?
- Q. 6.** Find the effective resistance of resistors 0.01 ohms and  $10^7$  ohms.in series and parallel
- Q. 7.** Two resistors of same materials has been connected in series first and then in parallel. Draw a V – I graph to distinguish these connection.
- Q. 8.** Three resistors 3,4,5 ohms are joined in parallel in a circuit. If a current of  $150 \text{ mA} = 150 \times 10^{-3} \text{ A}$  flows through the resistor of 4 ohms, then find the values of the current in mA which will be flowing in other two resistors?
- Q. 9.** A wire of length 2cm having resistance R is stretched to have an increase of 100% of original length . Find its new resistance with respect to its original resistance.
- Q. 10.** An electric lamp has resistance of 400 ohms. It is connected to a supply of 250V. If the price of electric energy is Rs.1.20 per unit, calculate the cost of lighting the lamp for 20 hours.