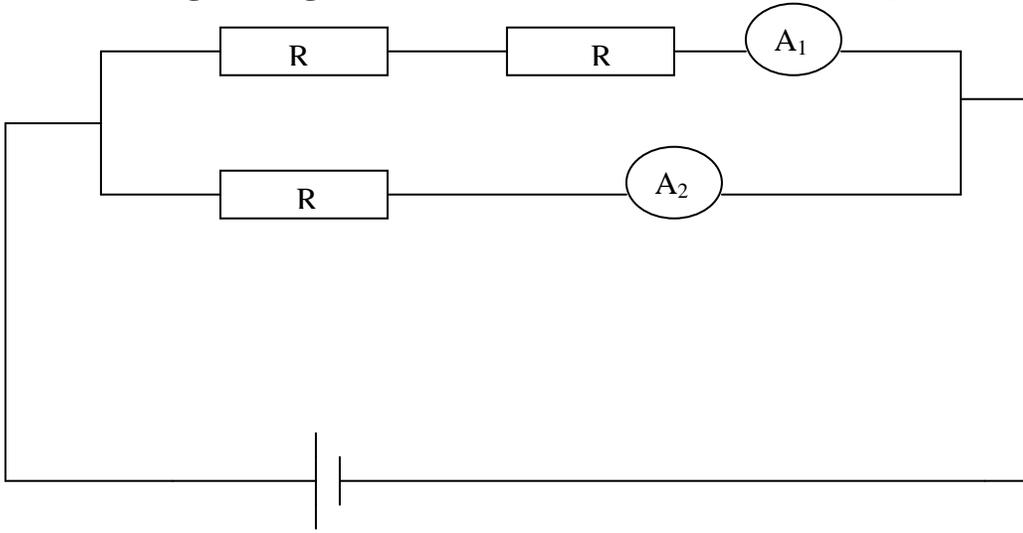


Chapter - 12
Electricity
(1 Mark Questions)

Q-1 In the given figure what is the ratio of current in A_1 , and A_2



Ans- $V=IR$ $V=\text{const.}$
 $I \propto 1/R$ $I_1/I_2 = R/2R$ $I_1/I_2 = 1/2$

Q-2 A wire of resistance R is bent in form of a closed circle, what is the resistance across a diameter of the circle?

Ans- $1/R' = 1/(R/2) + 1/(R/2)$ $R' = R/4.$

Q-3 A charge of 6 C is moved between two points P and Q having , potential 10V and 5V respectively. Find the amount of work done.

Ans- $W=q(V_2-V_1)=6(10-5)=30\text{ joule}$

Q-4 Name the physical quantity whose SI unit is JC^{-1} .

Ans-Potential

(2 Marks Questions)

Q-1 Two wires of equal cross sectional area , one of copper and other of manganin have same resistance. Which one will be longer?

Ans- $R=\rho L/A$ ($R,A=\text{const. } L=1/\rho$)

$\rho_{\text{manganin}} > \rho_{\text{copper}}$

$L_{\text{copper}} > L_{\text{manganin}}$

Q-2 A Rectangular block of iron has dimensions $L \times L \times b$. What is the resistance of the block measured between the two square ends ? Given $\rho =$ resistivity.

Ans- $R=\rho b/L^2$


Q-3 Three equal resistances are connected in series then in parallel. What will be the ratio of their Resistances?

Ans- $R_{\text{series}} = 3R$.

$$R_{\text{parallel}} = R/3$$

$$R_{\text{series}} / R_{\text{parallel}} = 3R / (R/3) = 9$$

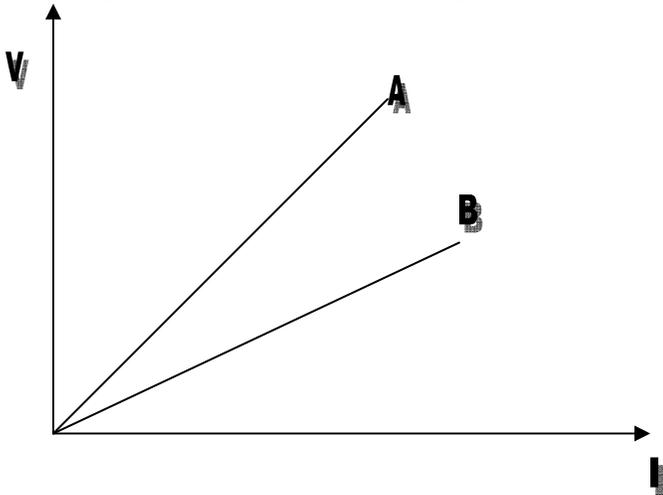Q-4 Jusitfy for any pair of resistance the equivalent resistance in series is greater equivalent resistance in parallel .



Ans- Since, $R = V/I$

$$R_A > R_B$$

A=Series, B=Parallel

Q-5 How many bulbs of 8Ω should be joined in parallel to draw a current of 2A from a battery of 4 V?

Ans- $R = V/I = 4/2 = 2\Omega$, let 'n' be the no of bulbs.

$$1/R = 1/R_1 + 1/R_2 + \dots + 1/R_n = n/8$$

$$1/2 = n/8, n=4.$$

Q-6 Two cubes A and B are of the same material. The side of B is thrice as that of A. Find the ratio R_A/R_B .

$$\text{Ans-} R_A = \rho L/A \quad R_B = \rho 3L/9A$$

$$R_A : R_B = 3:1$$

Q-7 3×10^{11} electrons are flowing through the filament of bulb for two minutes. Find the current flowing through the circuit. Charge on one electron = 1.6×10^{-19} C.

$$\text{Ans-} q = ne = 3 \times 10^{11} \times 1.6 \times 10^{-19} = 4.8 \times 10^{-8} \text{ C}$$

$$I = q/t = 4.8 \times 10^{-8} / (2 \times 60) = 4 \times 10^{-7} \text{ A}$$

Q-8 A nichrome wire of resistivity $100 \times 10^{-6} \text{ ohm-m}$ and copper wire of resistivity $1.62 \times 10^{-8} \text{ ohm-m}$ of same length and same area of cross section are connected in series, current is passed through them, why does the nichrome wire gets heated first?


Ans. $Q = I^2 R t$

$$Q = I^2 \left\{ \rho \frac{L}{A} \right\} t$$

Nichrome wire has higher resistivity than copper wire. Therefore, it is heated first

(3 Marks Questions)

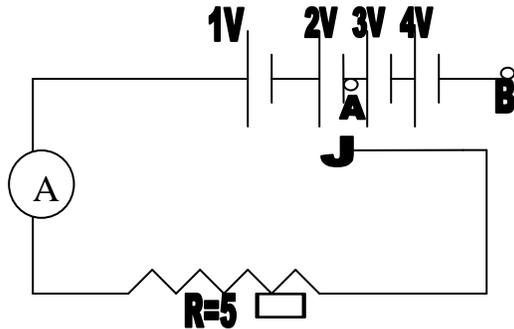Q1 In the given figure what is ratio of ammeter reading when J is connected to A and then to B



Ans. when J is connected to A

$$I = V/R = 3/5 \text{ A} = 0.6 \text{ A}$$

When J is connected to B

$$V = 1 + 2 + 3 + 4 = 10 \text{ V}$$

$$I = 10/5 = 2 \text{ A}$$