

10th Electricity – Remember these terms before solving Numerical problems

1. If a net charge Q , flows across any cross-section of a conductor in time t , then the current I , through the cross-section is

$$I = Q/t$$

$$Q = It$$

2. The electric potential difference between two points in an electric circuit carrying some current is the work done to move a unit charge from one point to the other –

Potential difference (V) between two points = Work done/Charge

$$V = W/Q$$

$$W = VQ$$

3. $Q = n \times$ Charge on 1 electron

When a steady current flows through a conductor, the electrons in it move with a certain average 'drift speed'.

4. If the current I , flowing in a metallic wire and the potential difference across its terminals is V .

Then potential difference, V , across the ends of a given metallic wire in an electric circuit is directly proportional to the current flowing through it, provided its temperature remains the same. This is called Ohm's law.

$$V \propto I \Rightarrow V = RI \quad \text{or, } I = V/R$$

5. Resistance of the conductor depends (i) on its length, (ii) on its area of cross-section, (iii) on the nature of its material and (iv) temperature

$$R \propto l/A \Rightarrow R = \rho l/A \quad \text{Or, } \rho = RA/l$$

6. If resistors joined in series: $V = V_1 + V_2 + V_3$ but $I = I_1 = I_2 = I_3$

$$\text{Then } R = R_1 + R_2 + R_3$$

6. If resistors joined in Parallel: $V = V_1 = V_2 = V_3$ but $I = I_1 + I_2 + I_3$

$$\text{Then } 1/R = 1/R_1 + 1/R_2 + 1/R_3$$

7. If a current I flowing through a resistor of resistance R . and the potential difference across is V for time t sec

Then, the work done in moving the charge Q through a potential difference V is $= W = VQ$.

But, $Q = It$

$$\Rightarrow W = V I t \quad \text{-----(i)}$$

Now, Power = work done / Time

$$\Rightarrow P = W/t$$

{or, $W = Pt$ [The energy supplied to the circuit by the source in time t is $P \times t = V I t$]

$$\Rightarrow P = V I t / t \quad \text{[Using eq. (i)]}$$

$$\Rightarrow P = VI \quad \text{----- (ii)}$$

The amount of heat produced in time $t = H$

$$\Rightarrow H = \text{the energy supplied to the circuit by the source in time } t = V I t$$

Applying Ohm's law, $V = IR$

$$H = I^2 R t$$

Note: heat produced in a resistor is

(i) Directly proportional to the square of current for a given resistance,

(ii) Directly proportional to resistance for a given current, and

(iii) Directly proportional to the time for which the current flows through the resistor.

8. Electric Power: The rate at which electric energy is dissipated or consumed in an electric circuit is called electric power.

The power P is given by $P = VI$ Using, $V = IR$

$$\Rightarrow P = I^2 R = V^2/R$$

Also using, $V/R = I$

$$\Rightarrow P = V^2/R$$

9. The commercial unit of electric energy is kilowatt hour (kW h) = 1 unit.

$$10. 1 \text{ kW h} = 1000 \text{ watt} \times 3600 \text{ second} = 3.6 \times 10^6 \text{ watt second} = 3.6 \times 10^6 \text{ joule (J)}$$